

## Seminar 12: Lectures 28-30

### Mutual Inductance:

1. Determine the mutual inductance per unit length between two long solenoids, one inside the other, whose radii are  $r_1$  and  $r_2$  ( $r_2 < r_1$ ) and whose turns per unit length are  $n_1$  and  $n_2$ . The value for the permeability of free space ( $\mu_0$ ) is  $4\pi \times 10^{-7} \text{ T} \cdot \text{m/A}$ .

### Self-Inductance:

2. There is a solenoid with an inductance 0.285 mH, a length of 36 cm, and a cross-sectional area  $6 \times 10^{-4} \text{ m}^2$ . (a) Find the number of turns of the solenoid. (b) Suppose at a specific time the emf is  $-12.5 \text{ mV}$ , find the rate of change of the current at that time.

Note you can use the following formula to calculate the inductance of a Solenoid  $L = \frac{\mu_0 N^2 A}{l}$



3. Ignoring any mutual inductance, what is the equivalent inductance of two inductors connected (a) in series, (b) in parallel?

### Magnetic Energy Storage:

4. Typical large values for electric and magnetic fields attained in laboratories are about  $1.0 \times 10^4 \text{ V/m}$  and  $2.0 \text{ T}$ . (a) Determine the energy density for each field and compare. (b) What magnitude electric field would be needed to produce the same energy density as the  $2.0 \text{ T}$  magnetic field? The value for the permeability of free space ( $\mu_0$ ) is  $4\pi \times 10^{-7} \text{ T} \cdot \text{m/A}$ , and the value for the permittivity of free space  $\epsilon_0$  is  $8.85 \times 10^{-12} \text{ C}^2/\text{N} \cdot \text{m}^2$ .

### LR Circuits:

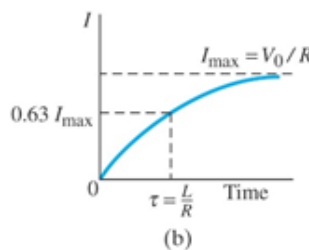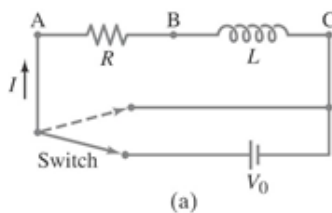5. After how many time constants does the current in the figure below reach within (a) 5.0%, (b) 1.0%, and (c) 0.10% of its maximum value?



### **LC Circuits and Oscillations:**

6. A 425-pF capacitor is charged to 135 V and then quickly connected to a 175 mH inductor. Determine (a) the frequency of oscillation, (b) the peak value of the current, and (c) the maximum energy stored in the magnetic field of the inductor.

### **LC Oscillations with Resistance:**

7. How much resistance must be added to a pure LC circuit ( $L = 350$  mH,  $C = 1800$  pF) to change the oscillator's frequency by 0.25%? Will it be increased or decreased?

### **AC Circuits; Reactance:**

8. What is the reactance of a 9.2  $\mu$ F capacitor at a frequency of (a) 60.0 Hz, (b) 1.00 MHz?
9. What is the inductance  $L$  of the primary of a transformer whose input is 110 V at 60 Hz and the current drawn is 3.1 A? Assume no current in the secondary.

### **LRC Series AC Circuit:**

10. For a 120 V, 60 Hz voltage, a current of 70 mA passing through the body for 1.0 s could be lethal. What must be the impedance of the body for this to occur?
11. A 75 W lightbulb is designed to operate with an applied ac voltage of 120 V rms. The bulb is placed in series with an inductor  $L$ , and this series combination is then connected to a 60 Hz 240 V rms voltage source. For the bulb to operate properly, determine the required value for  $L$ . Assume the bulb has resistance  $R$  and negligible inductance.

### **Resonance in AC Circuit:**

12. An LRC circuit has  $L = 4.15$  mH and  $R = 3.80$  k $\Omega$ . (a) What value must  $C$  have to produce resonance at 33.0 kHz? (b) What will be the maximum current at resonance if the peak external voltage is 136 V?