


Seminar 8: Resistors and Magnetism

Emf and Terminal Voltage:

1. Four 1.50 V cells are connected in series to a $12\ \Omega$ lightbulb. If the resulting current is 0.45 A, what is the internal resistance of each cell, assuming they are identical and neglecting the resistance of the wires?


Resistors in Series and Parallel:

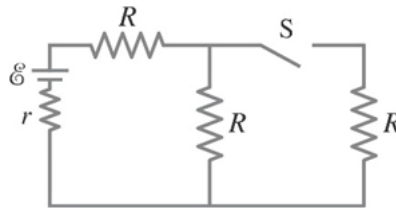2. Three $1.70\ \text{k}\Omega$ resistors can be connected together in four different ways, making combinations of series and/or parallel circuits. What are these four ways, and what is the net resistance in each case?
3. Three equal resistors (R) are connected to a battery as shown in the figure below. Qualitatively, what happens to (a) the voltage drop across each of these resistors, (b) the current flow through each, and (c) the terminal voltage of the battery, when the switch S is opened, after having been closed for a long time? (d) If the emf of the battery is 9.0 V, what is its terminal voltage when the switch is closed if the internal resistance r is $0.50\ \Omega$ and $R = 5.50\ \Omega$? (e) What is the terminal voltage when the switch is open?




Kirchoff's Rules:

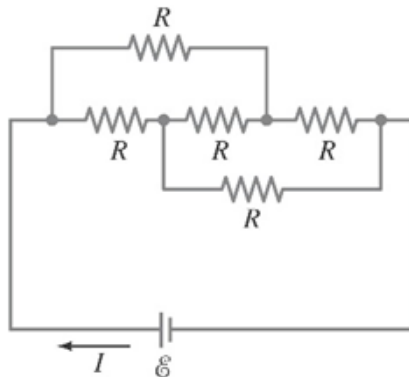4. (a) A network of five equal resistors R is connected to a battery \mathcal{E} as shown in the figure below. Determine the current I that flows out of the battery. (b) Use the value determined for I to find the single resistor R_{eq} that is equivalent to the five-resistor network.




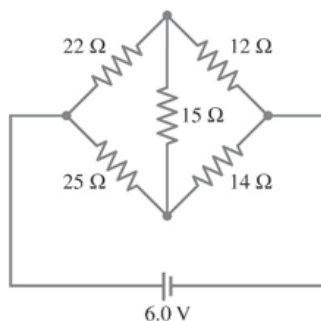5. Determine the current through each of the resistors in the figure below.



RC Circuits:

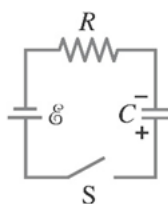6. In the figure below, the total resistance is $15.0\text{ k}\Omega$, and the battery's emf is 24.0 V . If the time constant is measured to be $24.0\text{ }\mu\text{s}$, calculate (a) the total capacitance of the circuit and (b) the time it takes for the voltage across the resistor to reach 16.0 V after the switch is closed.



7. How long does it take for the energy stored in a capacitor in a series RC circuit (shown in the figure above) to reach 75% of its maximum value? Express your answer in terms of the time constant $\tau = RC$?

Force on Electric Current in a Magnetic Field:

8. Calculate the magnitude of the magnetic force on a 240 m length of wire stretched between two towers and carrying a 150 A current. The Earth's magnetic field of $5.0 \times 10^{-5}\text{ T}$ makes an angle of 68° with the wire.
9. Suppose a straight 1.00 mm diameter copper wire could just 'float' horizontally in air because of the force due to the Earth's magnetic field \vec{B} , which is horizontal, perpendicular to the wire, and of magnitude $5.0 \times 10^{-5}\text{ T}$. What current would the wire carry? Does the answer seem feasible? Explain briefly.

Force on Charge Moving in a Magnetic Field:

10. An electron is projected vertically upward with a speed of $1.70 \times 10^6\text{ m/s}$ into a uniform magnetic field of 0.480 T that is directed horizontally away from the observer. Describe the electron's path in this field.
11. A 3.40 g bullet moves with a speed of 155 m/s perpendicular to the Earth's magnetic field of $5.00 \times 10^{-5}\text{ T}$. If the bullet possesses a net charge of $18.5 \times 10^{-9}\text{ C}$, by what distance will it be deflected from its path due to the Earth's magnetic field after it has traveled 1.00 km ?